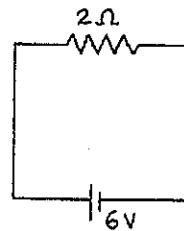


CONCEPTUAL *Physics* PRACTICE PAGE

Chapter 23 Electric Current Series Circuits

1. In the circuit shown at the right, a voltage of 6 V pushes charge through a single resistor of 2 Ω. According to Ohm's Law, the current in the resistor (and therefore in the whole circuit) is

_____ A.




THE EQUIVALENT RESISTANCE OF RESISTORS IN SERIES IS SIMPLY THEIR SUM!



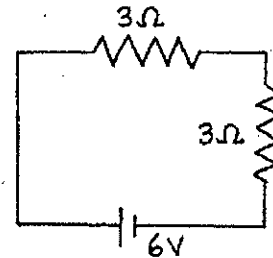2. Two 3-Ω resistors and a 6-V battery comprise the circuit on the right. The total resistance of the circuit is _____ Ω.

The current in the circuit is then _____ A.





3. The equivalent resistance of three 4-Ω resistors in series (not shown) is _____ Ω.

4. Does current flow *through* a resistor or *across* a resistor? _____

Is voltage established *through* a resistor or *across* a resistor? _____

5. Does current in the lamps of a circuit occur simultaneously or does charge flow first through one lamp, then the other, and finally the last in turn?

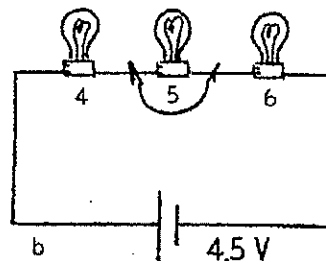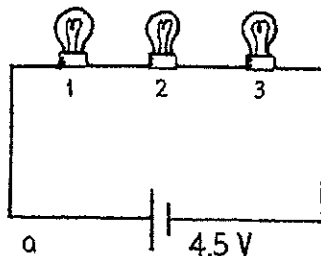6. Circuits *a* and *b* below are identical with all bulbs rated at equal wattage (therefore equal resistance). The only difference between the circuits is that bulb 5 has a short circuit, as shown.



a. In which circuit is the current greater?

b. In which circuit are all three bulbs equally bright?

c. Which bulb(s) is the brightest?










d. Which bulb(s) is the dimmest?

e. Which bulb(s) has the largest voltage drops across them?

f. Which circuit dissipates more power?

g. Which circuit produces more light?

PARALLEL CIRCUIT

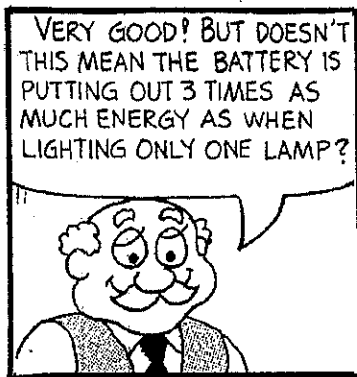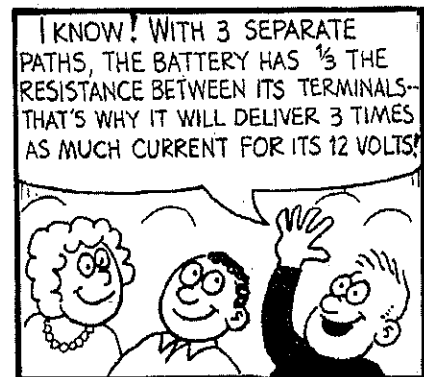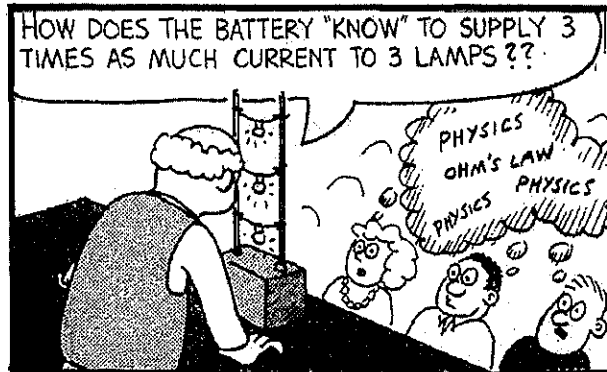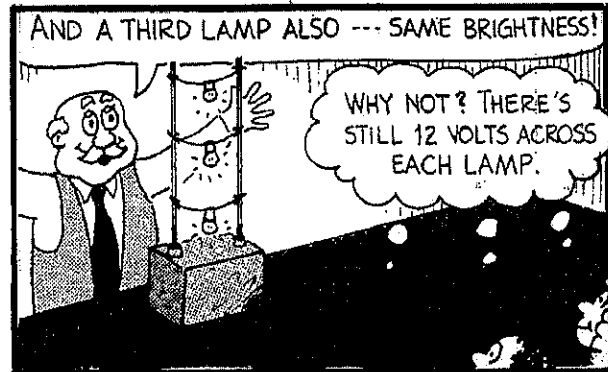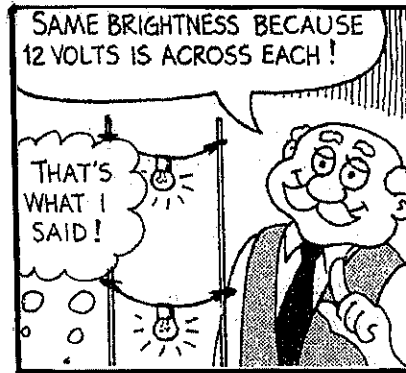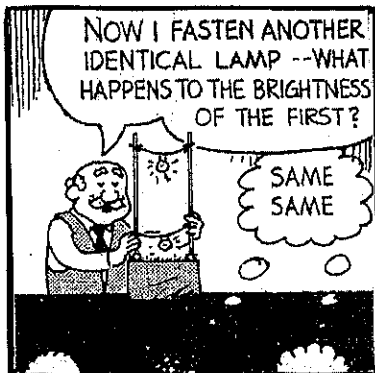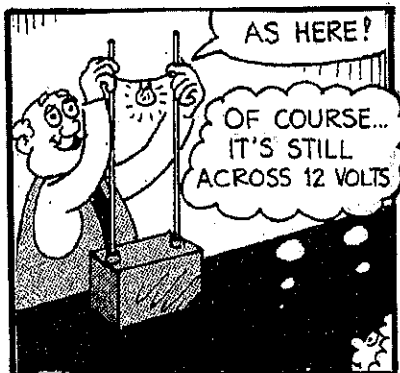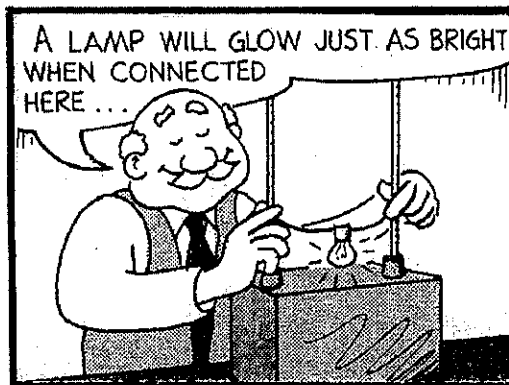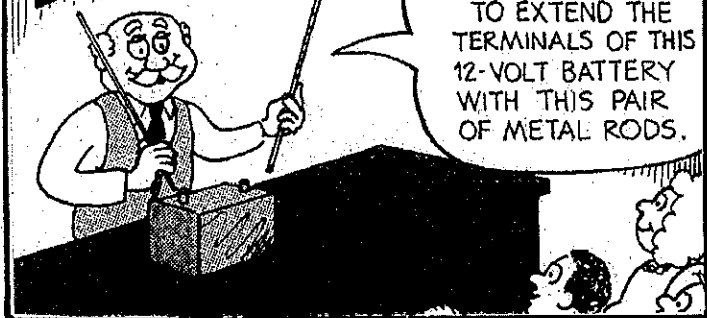


Hewitt
Drew it!

CONCEPTUAL *Physics* PRACTICE PAGE


Chapter 23 Electric Current Parallel Circuits

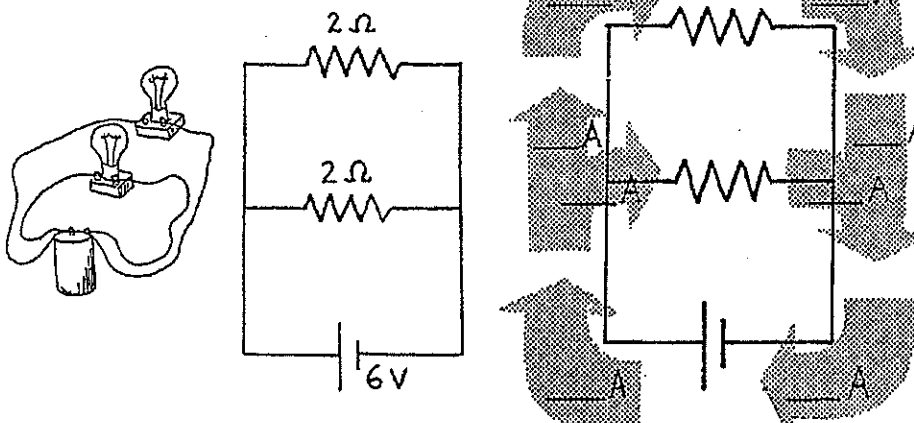1. In the circuit shown below there is a voltage drop of 6 V across *each* 2 Ω resistors.




- By Ohm's Law, the current in *each* resistor is _____ A.
- The current through the battery is the sum of the currents in the resistors, _____ A.
- Fill in the current in the eight blank spaces in the diagram above of the same circuit.

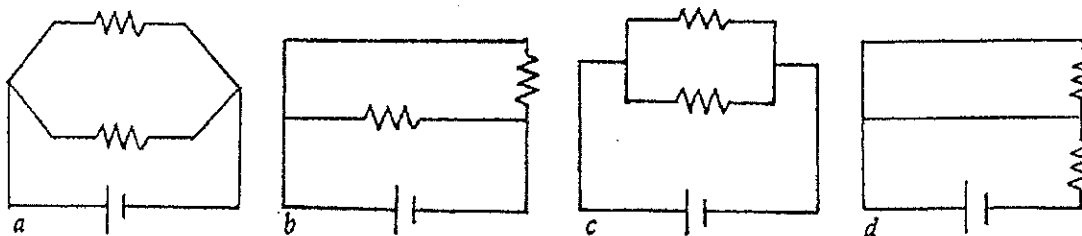2. Cross out the circuit below that is *not* equivalent to the circuit above.



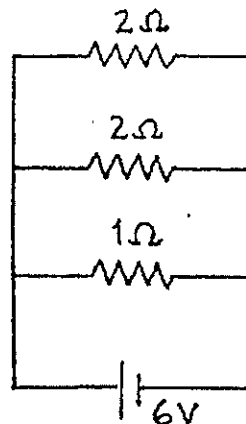3. Consider the parallel circuit at the right.

- The voltage drop across each resistor is _____ V.
- The current in each branch is:
 2-Ω resistor _____ A.
 2-Ω resistor _____ A.
 1-Ω resistor _____ A.
- The current through the battery equals the sum of the currents which equals _____ A.
- The equivalent resistance of the circuit equals _____ Ω.








THE EQUIVALENT RESISTANCE OF A PAIR OF RESISTORS IN PARALLEL IS THEIR PRODUCT DIVIDED BY THEIR SUM!

Hewitt
Draw it!

Chapter 23 Electric Current
Circuit Resistance

Figure what the resistances are, then show their values in the blanks to the left of each lamp.

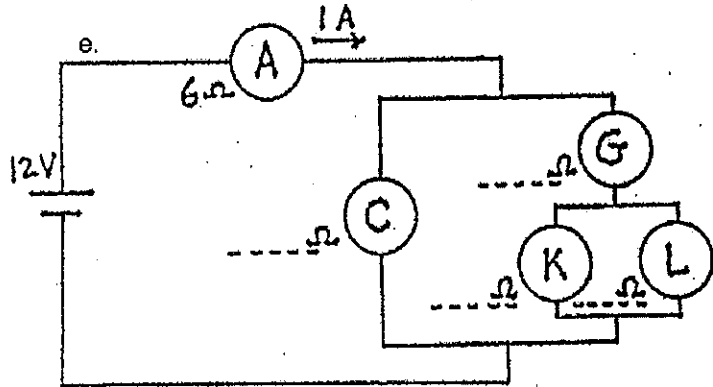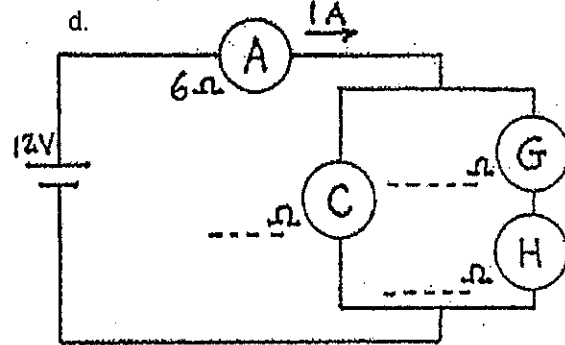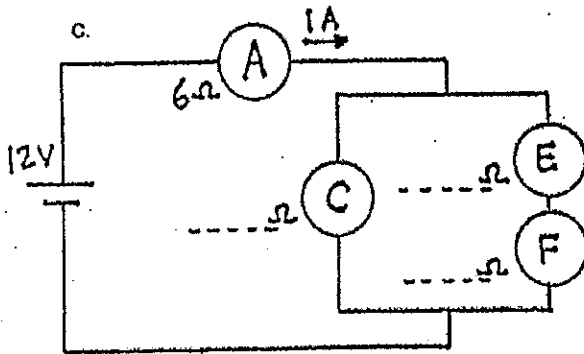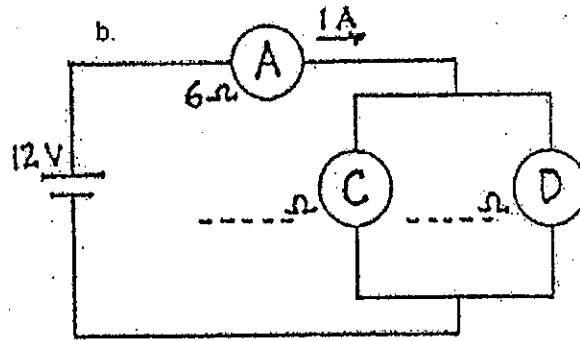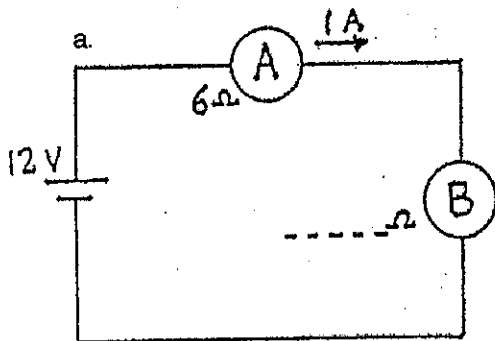All circuits below have the same lamp A with resistance of $6\ \Omega$ and the same 12-volt battery with negligible resistance. The unknown resistances of lamps B through L are such that the current in lamp A remains 1 ampere. Fill in the blanks.



Circuit a: How much current flows through the battery? _____ A.

Circuit b: Assume lamps C and D are identical. Current through lamp D is _____ A.

Circuit c: Identical lamps E and F replace lamp D. Current through lamp C is _____ A.

Circuit d: Lamps G and H replace lamps E and F, and the resistance of lamp G is twice that of lamp H. Current through lamp H is _____ A.

Circuit e: Identical lamps K and L replace lamp H. Current through lamp L is _____ A.

The equivalent resistance of a circuit is the value of a single resistor that will replace all the resistors of the circuit to produce the same load on the battery. How do the equivalent resistances of the circuits a through e compare?

Handy rule: For a pair of resistors in parallel:

$$\text{Equivalent resistance} = \frac{\text{product of resistances}}{\text{sum of resistances}}$$